

SECTION- A

Note: It contains 05 short answer type questions carrying 3 marks each. All the questions in this section are compulsory.

Q1: Three equal resistances of  $10\Omega$  are connected in delta. Calculate the resistance in one of the arms of an equivalent star circuit.

Q2: In a series RLC circuit, if C is increased, what happens to the resonant frequency?

Q3: Find the Laplace transform of function  $f(t) = \cos^2 5t$ .

Q4: Define transmission parameters A and B of a two-port network.

Q5: Discuss working of  $m$ -derived high pass filter.

SECTION- B

Note: -It contains 5 short answer type questions and each question carries 7 marks. All questions are compulsory.

Q1: Explain Millman's theorem with the help of suitable example.

Q2: Explain frequency response of a Parallel RLC circuit.

Q3: Explain the differentiation and integration property of Laplace transform.


Q4: Discuss the Z parameters of a two-port network.

Q5: Discuss in detail the principle and working of  $m$ -derived Low pass filter.


SECTION- C

Note: - It contains 5 long answer type questions carrying 15 marks each. Attempt any 2.

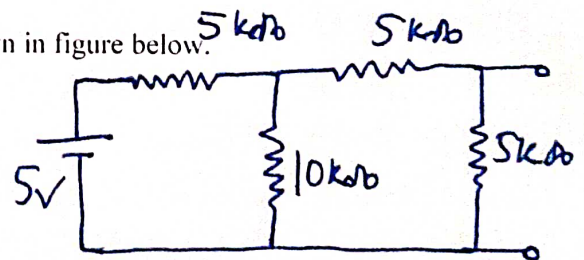Q1: Determine Norton's equivalent circuit for the given circuit shown in figure below.



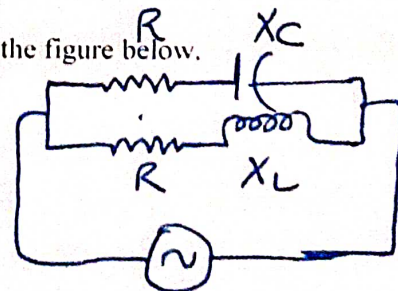Q2: Find the resonant frequency in the ideal parallel LC circuit shown in the figure below.



Q3: Determine the inverse Laplace transform of the function  $F(s) = \log(s^2-1)/s(s-1)$

Q4: If the parameters of a two port network are  $Z_{11} = 500\Omega$ ,  $Z_{22} = 700\Omega$ ,  $Z_{12} = Z_{21} = 300\Omega$ . Find the equivalent ABCD parameters.

Q5: Find an expression for the characteristic impedance and propagation constant of T network.